

3EJ4 LAB FIVE

McMaster University

Yichen Lu

400247938


luy191

November 25th, 2021

Questions for Part 1:

Q1.

(1)

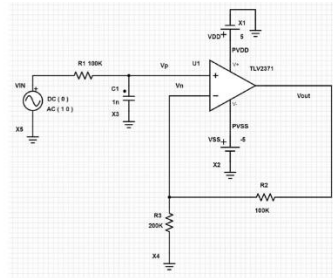

Yichen zu 400247938 10/19/1

$$(1) T(s) = \frac{V_o(s)}{V_{in}(s)}$$

$$\therefore V_+ = V_- \quad \therefore V_- = V_o(s) \frac{R_3}{R_2 + R_3} = V_+ \quad \text{*(Low frequency gain)} \\ \text{(when } s=0, \text{ we can get low-frequency gain)} \\ T(s=0) = A_v = 1 + \frac{R_2}{R_3} = 1 + 0.5 = 1.5 \approx 3.5 \text{ dB} \quad \text{(R}_2=100\text{k}, \text{R}_3=200\text{k}, \text{R}_1=100\text{k})$$

$$\therefore \frac{V_i(s) - V_+}{R_1} = \frac{V_+}{C_1 s} \quad \therefore \frac{V_i(s) - V_o(s) \frac{R_3}{R_2 + R_3}}{R_1} = V_o(s) \frac{R_3}{R_2 + R_3} C_1 s \quad \text{*(the -3dB frequency } f_c \text{)}$$

$$f_c = \frac{1}{2\pi R_1 C_1} = 1591 \text{ Hz} = 1.591 \text{ kHz} \quad \text{Cut off frequency}$$

$$\therefore \frac{V_o(s)}{V_{in}(s)} = \frac{R_2 + R_3}{R_3(R_1 s C_1 + 1)}$$

$$\therefore T(s) = \frac{R_2 + R_3}{R_3(R_1 s C_1 + 1)} \quad \text{(The transfer function)}$$

(2)

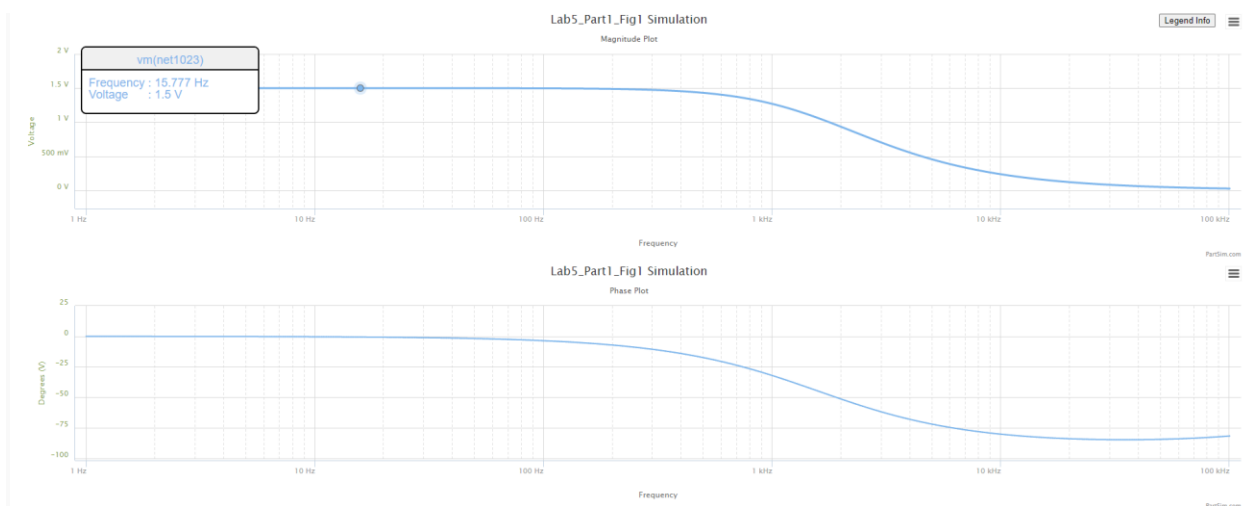


Figure 1(Transfer Function of the First order low pass filter)

3	1	1.500000172	-0.036069274			3	1	0.150733	-0.04738		
4	1.02305973	1.500000158	-0.036901021			4	1.023293	0.150697	-0.03871		
5	1.046651211	1.500000143	-0.037751948			5	1.047129	0.150725	-0.05035		
6	1.070786705	1.500000128	-0.038622498			6	1.071519	0.150721	-0.05976		
7	1.095478757	1.500000112	-0.039513122			7	1.096478	0.15074	-0.04839		
8	1.120740201	1.500000095	-0.040424284			8	1.122018	0.150721	-0.05523		
9	1.146584168	1.500000078	-0.041356456			9	1.148154	0.150721	-0.05791		
10	1.173024089	1.50000006	-0.042310125			10	1.174898	0.150733	-0.05753		
11	1.200073707	1.500000041	-0.043285784			11	1.202264	0.150766	-0.0554		
12	1.227747083	1.50000002	-0.044283942			12	1.230269	0.150736	-0.08636		
13	1.256058599	1.5	-0.045305118			13	1.258925	0.150673	-0.05251		

(Data for Av in Step 1.3)

(Data for Av in Step 1.8)

321	1407.715367	1.121597902	-41.50095622			307	1096.478	0.11406	-40.4487		
322	1440.176903	1.110238218	-42.14788529			308	1122.018	0.112948	-41.064		
323	1473.386993	1.098710673	-42.79617597			309	1148.154	0.111945	-41.7639		
324	1507.362899	1.087021837	-43.44549366			310	1174.898	0.11062	-42.4198		
325	1542.122281	1.075178653	-44.09550093			311	1202.264	0.109444	-43.0177		
326	1577.683204	1.06318842	-44.74585836			312	1230.269	0.108339	-43.7244		
327	1614.064152	1.051058766	-45.39622546			313	1258.925	0.107066	-44.4059		
328	1651.284035	1.038797632	-46.04626151			314	1288.25	0.105939	-44.9776		
329	1689.362199	1.02641324	-46.69562647			315	1318.257	0.104512	-45.7147		
330	1728.318435	1.013914073	-47.34398184			316	1348.963	0.103408	-46.2817		
331	1768.172991	1.001308839	-47.99099149			317	1380.384	0.102189	-47.025		
332	1808.946583	0.988606451	-48.63632259			318	1412.538	0.100867	-47.5719		
333	1850.660402	0.975815989	-49.27964637			319	1445.44	0.099675	-48.2746		
334	1893.336131	0.962946674	-49.92063896			320	1479.108	0.098333	-48.9631		
335	1936.995951	0.950007836	-50.55898215			321	1513.561	0.097076	-49.5829		

(Data for fc in Step 1.3)

(Data for fc in Step 1.8)

For the low-frequency gain, we can observe that V_{out} is 1.500000172V with $V_{in} = 1V$, computing, the low-frequency gain $A_v = 1.5/1 = 1.5 \text{ V/V}$ from its simulated data Step1.3. In terms of the measurement data, we can observe that V_{out} is 0.150733V with $V_{in} = 100mV$, computing, the low-frequency gain $A_v = 0.150733V / 100mV = 1.5 \text{ V/V}$ from its measured data Step1.8. These two A values are identical to the ones we estimated in Part 1 calculation.

For the -3dB frequency f_c , we can see that in Steps 1.3 and 1.8 that the simulated and measured values of f_c are 1614Hz and 1288.25Hz respectively given the data above,. The simulated value is a better match. This measurement mistake could be attributable to the amplifier's physical qualities.


Questions for Part 2:

Q2.

2.6, respectively.

Yichen Lu 400247938 1/19/1

Q2.

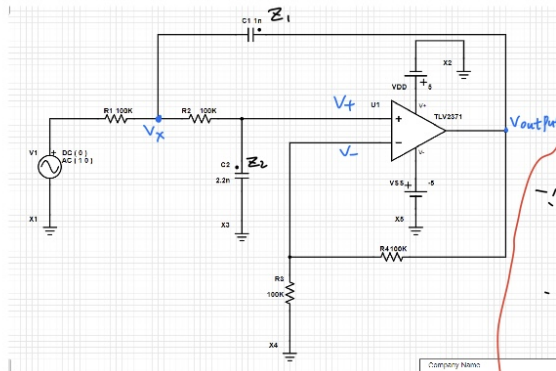

Transfer function:

$$T(s) = \frac{V_{out}(s)}{V_{in}(s)}$$

KCL at Node V_x :

$$\frac{V_x - V_{in}}{R_1} + \frac{V_x}{R_2 + Z_2} + \frac{V_x - V_{out}}{Z_1} = 0 \quad (1)$$

Voltage Division:

$$V_- = \frac{R_3}{R_3 + R_4} V_{out} = \frac{1}{2} V_{out} \quad (2)$$

Ideal op amp:

$$V_+ = V_- \quad (3)$$

Substitute V_x in (1)

$$\frac{V_{in}}{R} = \left(\frac{R + Z_1}{2Z_2R} + \frac{1}{2Z_2} + \frac{R - Z_2}{2Z_2Z_1} \right) V_{out}$$

$$\therefore \frac{V_{out}}{V_{in}} = T(s) = \frac{2Z_1Z_2}{R^2 + R(2Z_1 - Z_2) + Z_1Z_2}$$

$$\therefore T(s) = \frac{V_{out}(s)}{V_{in}(s)} = \frac{2 \cdot \frac{1}{s \cdot 1n} \cdot \frac{1}{s \cdot (2.2n)}}{(100k)^2 + 100k \cdot (\frac{2}{s \cdot 1n} - \frac{1}{s \cdot (2.2n)}) + \frac{1}{s \cdot 1n} \cdot \frac{1}{s \cdot (2.2n)}}$$

$$\therefore T(s) = \frac{\frac{1}{11} \times 10^8}{s^2 + \frac{17}{11} \times 10^4 \cdot s + \frac{1}{11} \times 10^8}$$

* Low-frequency gain (when $s=0$)

$$A_{low-f} = \frac{\frac{1}{11} \times 10^8}{\frac{1}{11} \times 10^8} = 2 \text{ V/V} = 20 \log 2 \text{ dB} \approx 6.02 \text{ dB}$$

	Hz	uV	uV				
3	1	6.020577025	-0.122644031	3	1	6.045335537	-0.110516861
4	1.02305973	6.020576448	-0.125472165	4	1.023292992	6.045384875	-0.11227988
5	1.046651211	6.020575844	-0.128365515	5	1.047128548	6.045768201	-0.10623526
6	1.070786705	6.020575212	-0.131325585	6	1.071519305	6.045115884	-0.1097998
7	1.095478757	6.020574551	-0.134353913	7	1.096478196	6.045379051	-0.11671016
8	1.120740201	6.020573859	-0.137452073	8	1.122018454	6.044316838	-0.11553917
9	1.146584168	6.020573134	-0.140621675	9	1.148153621	6.044502496	-0.11861858
10	1.173024089	6.020572376	-0.143864367	10	1.174897555	6.044317209	-0.11439544
11	1.200073707	6.020571583	-0.147181834	11	1.202264435	6.044304848	-0.11798997

(Data for A_v in Step 2.2)

(Data for A_v in Step 2.6)

The low frequency gain should be around 2 V/V, or roughly 6.02dB, according to the calculation in (1).

With $V_{in} = 1V = 0 \text{ dB}$, the output for simulation in step 2.2 is 6.020577025 dB. As a result, the low frequency gain is 6.020577025 dB, which is nearly identical to our calculation. The gain is 6.045335537 dB for step 2.6, which is fairly close to the value we intended (6.02 dB).

Q3.

Yichen Lu 400247938 14/9/

Q3.

Q3. (20 Points) Calculate (1) the pole frequency f_0 , (2) the cut-off frequency (or -3dB frequency) f_c , (3) the pole quality factor Q , (4) the peak value of the magnitude of the transfer function, and (5) the frequency f_{max} where the peak value of the magnitude of the transfer function happens. Verify the calculated results using the simulated data obtained in Step 2.2 and the measured data obtained in Step 2.6, respectively.

Yichen Lu 400247938 14/9/

$$(1) \because s^2 + \frac{17}{11} \times 10^4 s + \frac{5}{11} \times 10^8 = 0$$

$$\therefore s^2 + \frac{\omega_0}{Q} s + \omega_0^2 = 0$$

$$\therefore \omega_0^2 = \frac{5}{11} \times 10^8$$

$$f_0 = \frac{\omega_0}{2\pi} = \frac{\sqrt{\frac{5}{11} \times 10^8}}{2\pi} = 1.073 \text{ kHz}$$

$$\therefore Q = 0.33$$

$$(3) Q = 0.33$$

$$(4) \because |T(s)| \text{ to be maximum} \\ \therefore \text{denominator to be minimum}$$

$$\therefore \sqrt{\omega^2 + 3.273 \times 10^8 \omega + 2.966 \times 10^{15}} \text{ to be minimum}$$

$$\because \omega \geq 0 \therefore \omega = 0 = \omega_{max} \therefore |T(s)| = |T(s)|_{max}$$

$$\therefore |T(s)|_{max} = 2 \text{ V/V} = 6.02 \text{ dB}$$

$$(2) |T(j\omega_c)| = \frac{\sqrt{2}}{2} |T(j\omega)| ; \omega_c = 0$$

$$\left| \frac{A_0}{- \omega_c^2 + \frac{\omega_0 \omega_c}{Q} j + \omega_0^2} \right| = \frac{1}{\sqrt{2}} \cdot \frac{A_0}{\omega_0^2}$$

$$\therefore | - \omega_c^2 + 4.545 \times 10^7 + 2.045 \times 10^4 \omega_c j | \\ = \sqrt{2} \times 4.545 \times 10^7$$

$$\therefore [\omega_c^2 (-4.545 \times 10^7)^2 + (2.045 \times 10^4)^2 \omega_c^2] = 2 \times (4.545 \times 10^7)^2$$

$$\therefore \omega_c^2 \approx 6.19407 \times 10^6$$

$$\omega_c = 2488.79 \text{ rad/s}$$

$$\therefore f_c = \frac{\omega_c}{2\pi} = \frac{2488.79}{2\pi} = 396.1 \text{ Hz}$$

$$(5) f_{max} = \frac{\omega_{max}}{2\pi} = \frac{0}{2\pi} = 0 \text{ Hz}$$

(1) $f_0 = 1.073 \text{ kHz}$

(2) $f_c = 396.1\text{Hz}$

(3) $Q = 0.33$

(4) $|T(s)|_{\max} = 2V/V = 6.02\text{dB}$

(5) $f_{\max} = 0\text{Hz}$

DATA for q3	Calculated	Simulated	Measured
fo	1.073kHz	1070.78670498641Hz	954.992586021435Hz
fc	396.1Hz	401.754172617276Hz	436.515832240166Hz
Q	0.33	/	/
$ T(s) _{\max}$	6.02dB	6.020577025 dB	6.045335537 dB
fmax	0Hz	1	1

In conclusion, the calculated data is almost the same with the data from the simulated and measured data.

Questions for Part 3:

Q4.

Q4 Xichen Lu 40047938 14/9/21

∴ Ideal op-amp

∴ $V_- = V_+ = 0V$ (GND)

∴ KCL at V_x

$$\frac{V_x - V_{in}}{R} + \frac{V_x - V_{out}}{Z_C} + \frac{V_x - V_{out}}{Z_C + R} = 0 \quad (1)$$


∴ voltage division

$$\therefore \frac{V_x - 0}{Z_C} = \frac{0 - V_{out}}{R} \quad \therefore V_x = -\frac{Z_C}{R} V_{out} \quad (2)$$

Substitute (2) in (1)

$$\therefore \frac{V_{out}}{V_{in}} = -\frac{1}{\frac{Z_C}{R} + \frac{Z_C + R}{Z_C} + 1} = -\frac{1}{\frac{Z_C}{R} + \frac{R}{Z_C} + 2}$$
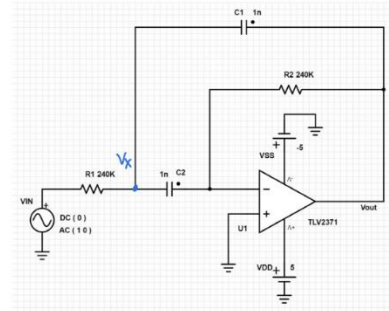
$$\therefore T(s) = \frac{V_{out}(s)}{V_{in}(s)} = -\frac{\frac{f}{12} \cdot 10^4 s}{(s + \frac{f}{12} \cdot 10^4)^2}$$



$$|T(s)| = \left| \frac{-\frac{f}{12} \cdot 10^4 s}{(s + \frac{f}{12} \cdot 10^4)^2} \right| = \left| \frac{\frac{f}{12} (10^4) j\omega}{(j\omega + \frac{f}{12} \cdot 10^4)^2} \right|$$

$$\text{Let } a = \frac{f}{12} \cdot 10^4$$

$$\therefore |T(s)| = \left| \frac{a j\omega}{(j\omega + a)^2} \right| = \frac{a\omega}{\sqrt{\omega^2 + a^2 + 2a\omega}} = \frac{a\omega}{\sqrt{(a^2 - \omega^2)^2 + (2a\omega)^2}}$$

$$= \frac{a\omega}{a^2 + \omega^2} \leq \frac{a}{\omega + a} = \frac{a}{2a} = \frac{1}{2} \quad (\text{when } \omega = a)$$

$$\therefore \text{center frequency gain } A_c = \frac{1}{2} V/V = -6.0206 \text{ dB}$$

Page 8

The center frequency gain is -6.02dB. From the calculation, we know that $\omega_0 = 41667 \text{ rad/s}$, then we can get $f_0 = \omega_0 / 2\pi = 663.15 \text{ Hz}$.

We can observe that the center frequency gain is 6.02058966 dB with frequency of 663.4102514 Hz from its simulated data Step3.2. In terms of the measurement data, we can observe that the center frequency gain is -5.56073747 dB with frequency of 501.1872336 Hz from its measured data Step3.6. These two values are identical to the ones we estimated in calculation.

Q5.

Q5. Yichen Lu 14/01 400247938

from Q4 we know

$$T(s) = \frac{4166.7s}{s^2 + 8333.3s + 4166.7^2}$$

when $\omega = \frac{1}{RC} = 4166.7 \text{ rad/s}$

when $\omega_0 = 4166.7 \text{ rad/s}$, $|T(s)|$ reaches its max

$$\therefore \left(s + \frac{1}{RC}\right)^2 = s^2 + \frac{2}{RC}s + \frac{1}{R^2C^2}$$

$$= s^2 + \frac{\omega_0}{Q}s + \omega_0^2$$

$$\therefore \begin{cases} \omega_0 = \frac{1}{RC} = 4166.7 \text{ rad/s} \\ Q = \frac{1}{2} \end{cases}$$

$\therefore p = -\frac{\omega_0}{2Q} \pm j\omega_0\sqrt{1 - \frac{1}{4Q^2}}$
 $\therefore p_1 = p_2 = -\frac{\omega_0}{2Q} = -4166.7$
 $\therefore \omega_{p1} = \omega_{p2} = 4166.7 \text{ rad/s}$
 $BW = \omega_{p2} - \omega_{p1} = 0$

(1) center frequency $\omega_0 = 4166.7 \text{ rad/s}$

(2) pole frequency factor $Q = 0.5$

(3) $\omega_{p1} = \omega_{p2} = 4166.7 \text{ rad/s}$

(4) 3-dB bandwidth $BW = 0$

Data for Q5	Calculated	Simulated	Measured
ω_0	4166.7 rad/s	$663.4102514 * 2\pi = 4168.3 \text{ rad/s}$	$501.1872336 * 2\pi = 3149.1 \text{ rad/s}$
Q	0.5	/	/

ω_{p1}	4166.7 rad/s	$663.4102514 * 2\pi = 4168.3$ rad/s	$501.1872336 * 2\pi = 3149.1$ rad/s
ω_{p2}	4166.7 rad/s	$663.4102514 * 2\pi = 4168.3$ rad/s	$501.1872336 * 2\pi = 3149.1$ rad/s
BW	0	0	0

In conclusion, the calculated data is almost the same with the data from the simulated and measured data.