

3EJ4 LAB ONE

McMaster University

Yichen Lu: 400247938

2021.9.25

Questions for Part 1(NPN-BJT 2N304):

According to the requirement, I got $I_C = 1.02 \cdot 10^{-3} \text{ A}$ and $V_{CE} = 1.898 \text{ V}$ from my table, Steps 1.2-1.4.

($V_E = -1.5 \text{ V}$, $V_{CC} = 0.5 \text{ V}$)

Q1.

(1) $V_{BEon} = 0.621 \text{ V}$ $I_B = 8.79 \text{ } \mu\text{A}$.

(2) Since $I_C = 1.02 \cdot 10^{-3} \text{ A}$

$$\beta = I_C / I_B = 1.02 \cdot 10^{-3} \text{ A} / 8.79 \text{ } \mu\text{A} = 117$$

(3) $|V_A| = 1000 \text{ V}$

(4) $r_o = 976 \text{ K}\Omega$

(5) $g_m = 41 \text{ mS}$

(6) $r_\pi = 2.845 \text{ K}\Omega$

Q2.

According to the requirement, I got $I_C = 1.59 \cdot 10^{-3} \text{ A}$ and $V_{CE} = 3.3408 \text{ V}$ from my table, Steps 1.8. (NPN-BJT 2N304)

(1) $I_C = 1.59 \text{ mA}$

(2) $V_{BEon} = 0.653 \text{ V}$ $I_B = 8.47 \text{ } \mu\text{A}$

(3) Since $I_C = 1.59 \cdot 10^{-3} \text{ A}$

$$\beta = I_C / I_B = 1.59 \cdot 10^{-3} \text{ A} / 8.47 \text{ } \mu\text{A} = 187.72$$

(4) $|V_A| = 75 \text{ V}$.

(5) $r_o = 47.1 \text{ kohm}$

(6) $g_m = 63.7 \text{ mS}$

(7) $r_\pi = 2.952 \text{ K}\Omega$

Q3.

Questions for Part 2(PNP-BJT 2N306):

According to the requirement, I got $I_C = 1.03 \cdot 10^{-3} \text{ A}$ and $V_{EC} = 1.90 \text{ V}$ from my table, Steps 2.2-2.4.

($V_E = -1.5 \text{ V}$, $V_{CC} = 0.5 \text{ V}$)

(1) $V_{BEon} = 0.660 \text{ V}$ $I_B = 8.40 \text{ }\mu\text{A}$.

(2) Since $I_C = 1.03 \cdot 10^{-3} \text{ A}$

$$\beta = I_C / I_B = 1.03 \cdot 10^{-3} \text{ A} / 8.40 \text{ }\mu\text{A} = 122.62$$

(3) $|V_A| = 143 \text{ V}$.

(4) $r_o = 139 \text{ K}\Omega$

(5) $g_m = 41.2 \text{ mS}$

(6) $r_\pi = 2.976 \text{ K}\Omega$

Q4.

According to the requirement, I got $I_C = 1.82 \cdot 10^{-3} \text{ A}$ and $V_{EC} = 1.82 \text{ V}$ from my table, Steps

1.8. (PNP-BJT 2N306)

(1) $I_C = 1.82 \text{ mA}$

(2) $V_{BEon} = 0.669 \text{ V}$. $I_B = 8.31 \text{ }\mu\text{A}$.

(3) Since $I_C = 1.82 \cdot 10^{-3} \text{ A}$

$$\beta = I_C / I_B = 1.82 \cdot 10^{-3} \text{ A} / 8.31 \mu\text{A} = 219.01$$


$$(4) |V_A| = 28 \text{ V.}$$

$$(5) r_o = 15.6 \text{ K}\Omega$$

$$(6) g_m = 72.8 \text{ mS}$$

$$(7) r_\pi = 3.008 \text{ K}\Omega$$

Q5.

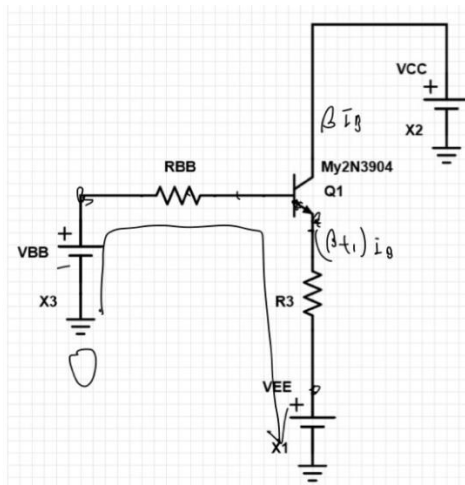

Yichen Lu, 400247938, 10/1/21
Sep. 23rd, 2021

$$0 + V_{BB} - I_B \cdot R_{BB} - V_{BE_{on}} - (\beta + 1) I_B \cdot R_3 - V_{EE} = 0$$

$$-I_B (R_{BB} + (\beta + 1) R_3) = V_{EE} - V_{BB} + V_{BE_{on}}$$

$$I_B = \frac{-(V_{EE} - V_{BB} + V_{BE_{on}})}{(R_{BB} + (\beta + 1) R_3)}$$

Q6. (compared to the I_B expression obtained in Q5 with (1.3),

$$(1.3): I_B = \frac{V_{BB} - (V_{EE} + V_{BE(on)})}{R_{BB}} \quad (Q5): I_B = \frac{-(V_{EE} - V_{BB} + V_{BE(on)})}{(R_{BB} + (\beta + 1)R_3)}$$

The difference is that the equation derived in Q5 has an additional $(\beta + 1)R_3$ in the denominator.

If ΔV_{EE} is applied,

* Using (1.3),

$$\begin{aligned} \Delta I_{B1} = I_{B1}' - I_{B1} &= \frac{V_{BB} - (V_{EE} + \Delta V_{EE} + V_{BE(on)})}{R_{BB}} - \frac{V_{BB} - (V_{EE} + V_{BE(on)})}{R_{BB}} \\ &= \frac{-\Delta V_{EE}}{R_{BB}} \end{aligned}$$

* Using the equation in Q5,


$$\begin{aligned} \Delta I_{B2} = I_{B2}' - I_{B2} &= \frac{V_{BB} - (V_{EE} + \Delta V_{EE} + V_{BE(on)})}{R_{BB} + (\beta + 1)R_3} - \frac{V_{BB} - (V_{EE} + V_{BE(on)})}{R_{BB} + (\beta + 1)R_3} = \frac{-\Delta V_{EE}}{R_{BB} + (\beta + 1)R_3} \\ |\Delta I_{B2}| - |\Delta I_{B1}| &= \Delta V_{EE} \left(\frac{1}{R_{BB} + (\beta + 1)R_3} - \frac{1}{R_{BB}} \right) = \Delta V_{EE} \cdot \frac{-(\beta + 1)R_3}{R_{BB}(R_{BB} + (\beta + 1)R_3)} < 0 \end{aligned}$$

Hence $|\Delta I_{B2}| < |\Delta I_{B1}|$ $\therefore R_3$ reduces ΔI_B when there is a ΔV_{EE} applied.

Yichen Lu 400247938 10/19/21

Sep. 23rd, 2021

Q7:

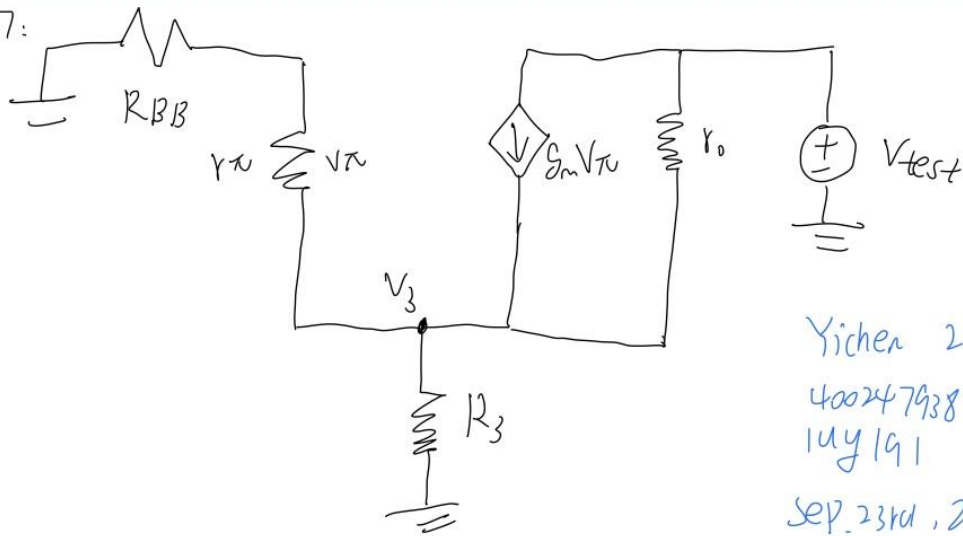

Yichen zu

400247938

14y191

Sep. 23rd, 2021

$$V_3 = [(R_{BB} + r_{\pi}) \parallel R_3] \cdot I_{test}$$

$$I_{test} = g_m V_{\pi} + \frac{V_{test} - V_3}{r_o}$$

$$V_{\pi} = -[(R_{BB} + r_{\pi}) \parallel R_3] \cdot I_{test} \cdot \frac{r_{\pi}}{r_{\pi} + R_{BB}}$$

$$I_{test} = -g_m [(R_{BB} + r_{\pi}) \parallel R_3] \cdot I_{test} \cdot \frac{r_{\pi}}{r_{\pi} + R_{BB}} + \frac{V_{test} - [(R_{BB} + r_{\pi}) \parallel R_3] \cdot I_{test}}{r_o}$$

$$I_{test} = -g_m [(R_{BB} + r_{\pi}) \parallel R_3] \cdot I_{test} \cdot \frac{r_{\pi}}{r_{\pi} + R_{BB}} + \frac{V_{test}}{r_o} - \frac{[(R_{BB} + r_{\pi}) \parallel R_3] \cdot I_{test}}{r_o}$$


$$I_{test} + g_m [(R_{BB} + r_{\pi}) \parallel R_3] \cdot I_{test} \cdot \frac{r_{\pi}}{r_{\pi} + R_{BB}} + \frac{[(R_{BB} + r_{\pi}) \parallel R_3] \cdot I_{test}}{r_o} = \frac{V_{test}}{r_o}$$

$$I_{test} \left\{ 1 + g_m [(R_{BB} + r_{\pi}) \parallel R_3] \cdot \frac{r_{\pi}}{r_{\pi} + R_{BB}} + \frac{[(R_{BB} + r_{\pi}) \parallel R_3]}{r_o} \right\} = \frac{V_{test}}{r_o}$$

$$\therefore \frac{V_{test}}{I_{test}} = r_o + [(R_{BB} + r_{\pi}) \parallel R_3] + g_m [(R_{BB} + r_{\pi}) \parallel R_3] \cdot r_o \cdot \left[\frac{r_{\pi}}{r_{\pi} + R_{BB}} \right]$$

$$\therefore R_o = r_o + [R_3 \parallel (R_{BB} + r_{\pi})] \left[1 + g_m r_o \left(\frac{r_{\pi}}{R_{BB} + r_{\pi}} \right) \right]$$

Q 8:

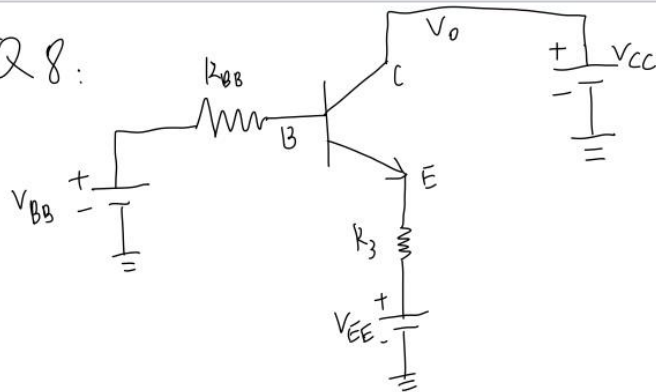

Sichen zu

400247938

14.1.91

Sep. 23rd, 2021

$$\therefore V_O = V_{CC}$$

$$\therefore V_{O, \min} = V_E + 0.3V \quad (\text{according to part 3/4}),$$

\therefore BJT works in active region

$$V_{O, \min} = V_E + 0.3V$$

$$= V_{EE} + V_E + 0.3V$$

$$= V_{EE} + (\beta + 1)I_B R_E + 0.3V$$

$$= \left[V_{EE} + (\beta + 1)R_E \frac{V_{BB} - V_{EE} - V_{BE, \min}}{R_{BB} + (\beta + 1)R_E} + 0.3V \right]$$

$$\therefore V_{O, \min} = V_{EE} + I_E R_E + 0.3V$$

Q9, $\because V_{EE} = -5V$, $I_o = 1mA = I_C$, $V_{o,min} = -1V$ $\beta = 117$ (from Q1)
 $R_2 = 100k\Omega$, $V_{CE} = 0.3V$

$$\therefore V_{o,min} = V_{EE} + I_E R_3 + 0.3V$$

$$\therefore \frac{I_C (\beta + 1)}{\beta} = I_E$$

$$\therefore R_3 = \frac{V_3}{I_3} = \frac{V_{o,min} - V_{EE} - V_{CE}}{I_E} = \frac{V_{o,min} - V_{EE} - V_{CE}}{\frac{I_C (\beta + 1)}{\beta}} = \frac{(-1V) - (-5V) - 0.3}{1mA(117+1)}$$

$$\therefore R_3 = (-1 - 0.3 + 5) / (1 \cdot \frac{118}{117}) k\Omega = \boxed{3.669 k\Omega}$$

$$\therefore R_{BB} = \frac{R_1 R_2}{R_1 + R_2}, \quad V_{BB} = \frac{R_1}{R_1 + R_2} V_{EE}, \quad \therefore V_{BB} = R_{BB} \cdot \frac{V_{EE}}{R_2}$$

$$\therefore V_{o,min} = V_{EE} + (\beta + 1) R_3 \frac{V_{BB} - V_{EE} - V_{BE(on)}}{R_{BB} + (\beta + 1) R_3} + 0.3$$

$$\therefore \frac{V_{BB} - V_{EE} - V_{BE(on)}}{R_{BB} + (\beta + 1) R_3} = \frac{V_{o,min} - V_{EE} - 0.3}{(\beta + 1) R_3}$$

$$\frac{R_{BB} \cdot \frac{V_{EE}}{R_2} - V_{EE} - V_{BE(on)}}{R_{BB} + (\beta + 1) R_3} = \frac{V_{o,min} - V_{EE} - 0.3}{(\beta + 1) R_3}$$

$$\frac{R_{BB} \cdot \frac{-5}{100} + 5 - 0.621}{R_{BB} + 118 \times 3.669} = \frac{-1 + 5 - 0.3}{118 \times 3.669}$$

$$-\frac{1}{20} R_{BB} + 4.379 = 8.5462 \times 10^{-2} \cdot R_{BB} + 3.7$$

$$\therefore R_{BB} = 11.5977 k\Omega$$


$$\therefore R_{BB} = \frac{R_1 R_2}{R_1 + R_2} \quad \therefore R_1 = \frac{1}{\frac{1}{R_{BB}} - \frac{1}{R_2}} = \frac{1}{\frac{1}{11.5977} - \frac{1}{100}} = \boxed{13.12 k\Omega}$$

Yichen Lu


400247938

1ug191

Sep. 23rd 2021

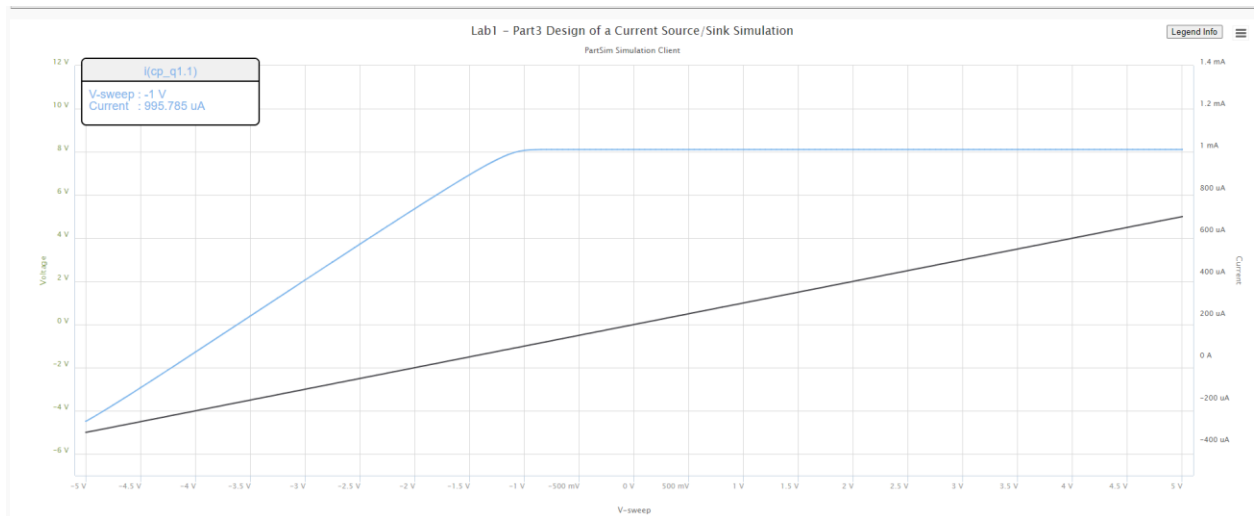

Q10

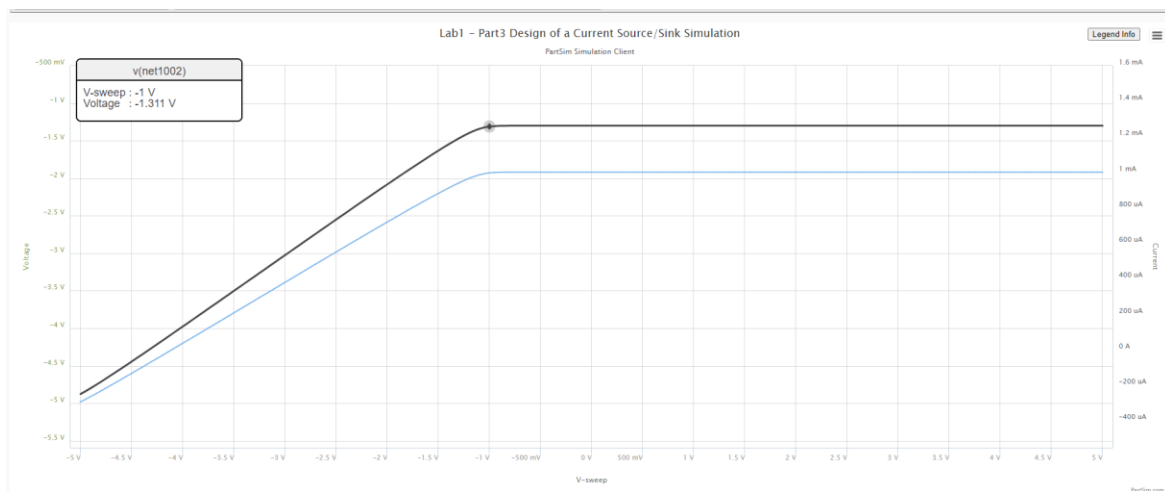

As the figure shown, the difference between V_C and V_E is $-1V - (-1.311V) = 0.311V$ which is close to $0.3V$ as I_C turns into the active region. Hence, this result determines that our assumption for $|V_{CE}| \geq 0.3V$ for Q1 to work in the active region is correct.