

McMaster University

Electrical and Computer Engineering Department

EE3EJ4 Electronic Devices and Circuits II - Fall 2021



Lab. 3 Multi-Stage Amplifiers

Lab Report Due on Oct. 31, 2021

Objective: To characterize BJT-based a common-collector (CC) amplifier, a current mirror and use them to design a multi-stage differential amplifier for high-gain applications.

Attributes Evaluated: These are the attributes you need to demonstrate in your solutions.

- Competence in specialized engineering knowledge to simulate circuit performance using SPICE-based circuit simulator and conduct analog circuit debugging;
- Ability to obtain substantiated conclusions as a result of a problem solution, including recognizing the limitations of the approaches and solutions; and
- Ability to assess the accuracy and precision of results.

Test Equipment:

- Analog Discovery 2 (AD2)
- [WaveForms from Digilent Link](#)
- [Analog Discovery 2 Quick Start Series Videos](#)
- [WaveForms Reference Manual](#)

Components:

- Transistors: $5 \times$ NPN-BJT 2N3904 $2 \times$ PNP-BJT 2N3906
- Resistors: $2 \times$ 76.8 k Ω resistor $2 \times$ 57.6 k Ω resistor $2 \times$ 8.06 k Ω resistor

Transistors in the circuit:

For a detailed description of these transistors, please check the following websites:

<https://www.onsemi.com/products/discretes-drivers/general-purpose-and-low-vcesat-transistors/2n3904>
or <https://www.onsemi.com/pub/Collateral/2N3903-D.PDF>

<https://www.onsemi.com/products/discretes-drivers/general-purpose-and-low-vcesat-transistors/2n3906>
or <https://www.onsemi.com/pub/Collateral/2N3906-D.PDF>

Reminder: Switch off the DC power suppliers first whenever you need to change the circuit configurations. Switch on the DC power suppliers only when you don't have to change the circuit connection anymore.

Part 1: Common-Collector (CC) Amplifier/Emitter Follower

A. Pre-lab Simulation

- 1.1 In [PartSim](#) (or [LTspice](#)), construct the CC amplifier, as shown in Fig. 1, using an NPN-BJT 2N3904 and the current sink characterized in Fig. 3. Here V_{sig} provides the required DC bias for Q_2 and the AC signal for the CC amplifier.
- 1.2 **DC Characteristics:** Sweep the DC voltage of V_{sig} , from -5 V to 5V with 0.5 V step, and measure the output voltage V_o at the emitter of Q_2 and the emitter current I_{E2} of Q_2 , respectively. Record the simulated V_o and I_{E2} in the sheet “Step 1.2” of the Excel file “Lab 3 – Multi-Stage Amplifier.xlsx”. Mark the DC value of $V_{sig} = V_{BQ2}$ which results in $V_o \approx 0V$.
- 1.3 **Frequency Response:** Set the DC value of $V_{sig} = V_{BQ2}$ and the AC amplitude of $V_{sig} = 1$ mV, conduct AC analysis for V_o in DEC with Start Frequency = 100 Hz, Stop Frequency = 1 MHz, and Total Points Per Decade = 101. Choose REAL for magnitude unit and degree (DEG) for phase unit. Record the simulated magnitude and phase of V_o in the sheet “Step 1.3” of the Excel file “Lab 3 – Multi-Stage Amplifier.xlsx”.

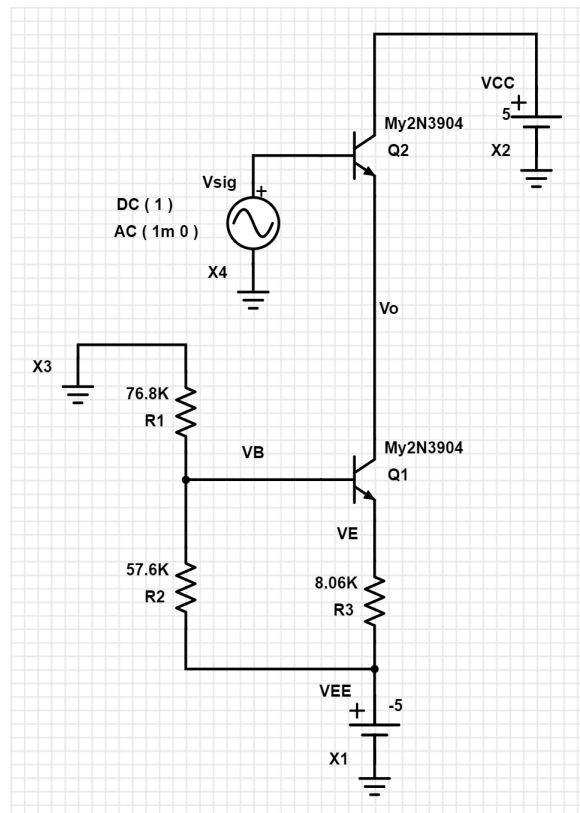


Fig. 1 Schematic diagram of the common-collector (CC) amplifier

B. In-lab Measurement

- 1.4 Based on Fig. 1, construct the measurement setup for the common-collector (CC) amplifier. Use $V^+ = 5\text{V}$ for V_{CC} , $V^- = -5\text{V}$ for V_{EE} , and Wavegen 1 (W1) for V_{sig} . Connect GNDV+, GNDV-, and GNDW1 to a common ground line.
- 1.5 Connect Scope Ch. 1 Positive (1+) to V_{sig} at the base of Q_2 and Scope Ch. 2 Positive (2+) to V_o at the emitter of Q_2 . Connect Scope Ch. 1 Negative (1-) and Scope Ch. 2 Negative (2-) to the common ground.
- 1.6 **DC Characteristics:** In WaveForms, click Workspace, open the provided workspace script “Lab3_Step1.6.dwf3work” and press Run. This script will sweep the DC voltage of Wavegen 1 (W1) from -5 V to 5 V with a 0.5 V step and measure the input voltage V_{sig} at the base of Q_2 and the output voltage V_o at the emitter of Q_2 , respectively. Record the measured V_{sig} and V_o in the sheet “Step 1.6” of the Excel file “Lab 3 – Multi-Stage Amplifier.xlsx”.
- 1.7 **AC Voltage Gain:** In WaveForms, click Workspace, open the provided workspace script “Lab3_Step1.7.dwf3work” and press Run. This script will enable Channel 1 (W1), set the Type = Sine, Frequency = 100 Hz, Amplitude = 1 mV (Note: in theory, the amplitude cannot exceed $0.2V_T = 5\text{ mV}$), Symmetry = 50%, and Channel 1 (W1) Phase = 0° . It returns the voltage gain A_v . It also finds the $V_{sig} = V_{BQ2}$ to result in $V_o \approx 0\text{ V}$ and sets the offset voltage of W1 accordingly.
- 1.8 **Using Scopes:** Display the measurement results using the Scope function in WaveForms. Use Y Cursors to set their upper and lower peak values and use the Ref function to calculate the difference. Record the measured amplitudes of Scope Ch. 1 Positive (1+) and Scope Ch. 2 Positive (2+) in the sheet “Step 1.8” of the Excel file “Lab 3 – Multi-Stage Amplifier.xlsx” to calculate the voltage gain A_v in dB. Copy and paste the screenshot of the measurement results to replace the one in the sheet “Step 1.8” of the Excel file “Lab 3 – Multi-Stage Amplifier.xlsx” to support your calculation. Make sure to capture the date and time of your PC in the screenshot.
- 1.9 Disconnect the circuit from the power supply V_{CC} , but keep the rest of the CC amplifier circuit connected. We will use it again in Lab 4 when we design a directly coupled operational amplifier.

C. Questions for Part 2:

For the common collector (CC) amplifier characterized, answer the following questions with simulated and measured data and discuss any discrepancy between the simulation and measurement results.

Q1. (15 Points) Based on the simulation and measurement data obtained in Steps 1.2 and 1.6, (1) plot the simulated and measured V_o vs. V_{sig} characteristics and discuss/justify the characteristics. (2) To ensure the circuit work as a common-collector (CC) amplifier, find the DC input range for V_{sig} and the output voltage range for V_o . (3) Find the V_{sig} value that results in $V_o \approx 0\text{ V}$.

Q2. (10 Points) Based on the simulation and measurement data obtained in Steps 1.3 and 1.8, what are the simulated and measured intrinsic voltage gain A_{vo} at low frequency (i.e., 100 Hz) of this CC amplifier? Report its magnitude in dB and phase in degree.

Part 2: Differential Amplifier with Current Mirror (CM) Load

A. Pre-lab Simulation – DC Analysis of a Current Mirror

- 2.1 The current mirror transfers the AC signal from one side of a differential pair to the output port. To characterize a current mirror, construct the circuit in [PartSim](#) (or [LTspice](#)) with the resistance value and supply voltages, as shown in Fig. 2. Here the current source I_{REF} represents the reference current to be transferred, and the R_L represents the load at the output of the current mirror.
- 2.2 **DC Characteristics:** Sweep I_{REF} from 0.1 mA to 1 mA with 0.01 mA current step, measure the output current I_o , which is the current flowing into the resistor R_L , and the voltages V_{in} and V_o at the collectors of Q1 and Q2, respectively. Record the simulated I_{REF} , I_o , V_{in} , and V_o in the sheet “Step 2.2” of the Excel file “Lab 3 – Multi-Stage Amplifier.xlsx”.
- 2.3 **Quiescent (Q-) Point Characterization:** Sweep I_{REF} from 85 μ A to 95 μ A with 0.1 μ A current step, measure the output current I_o , which is the current flowing into the resistor R_L , and the voltages V_{in} and V_o at the collectors of Q1 and Q2, respectively. This sweeping range corresponds to the designed bias current of the transistor in the differential-pair amplifier. Record the simulated I_{REF} , I_o , V_{in} , and V_o in the sheet “Step 2.3” of the Excel file “Lab 3 – Multi-Stage Amplifier.xlsx”.

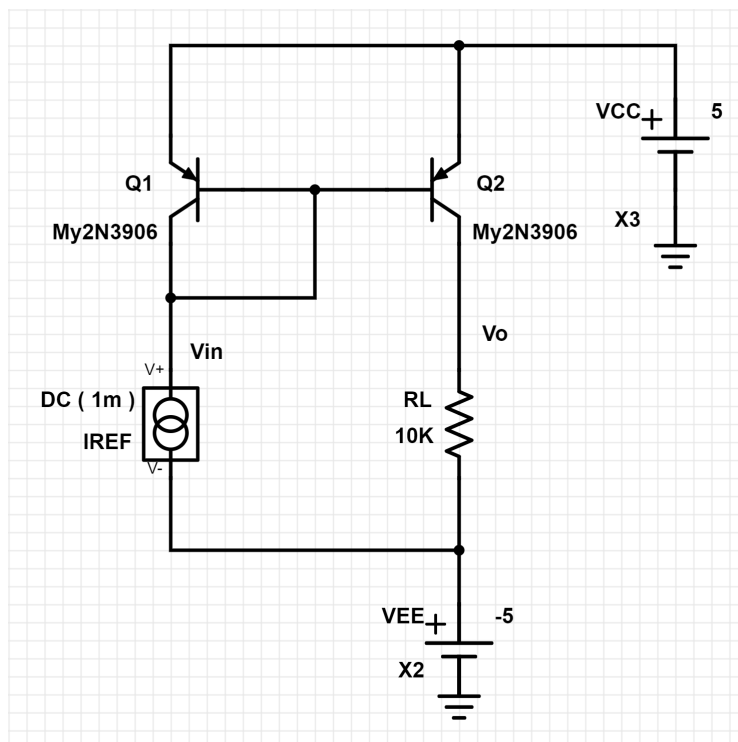


Fig. 2 Schematic diagram of the current mirror for the DC analysis

B. Pre-lab Simulation – AC Analysis of a Current Mirror

- 2.4 Construct the circuit, as shown in Fig. 3, in [PartSim](#) (or [LTspice](#)). Here C_2 is a dummy bypass capacitor with 100 TF, and V_2 is a dummy AC voltage source as the port 2 stimulus used in the AC analysis.
- 2.5 **Current Gain & Input Impedance:** Set the DC value of $I_{REF} = 91.0 \mu\text{A}$ (the DC current of each differential pair amplifier in Part 1.C) and its AC value to $1 \mu\text{A}$. Set the DC and AC voltages of V_2 equal to zero. Conduct AC analysis to measure V_{in} and I_2 (taken from the negative terminal of C_2) in LIN with start frequency = 100 Hz, stop frequency = 200 Hz, and 11 frequency points in total. Choose REAL for magnitude unit and degree (DEG) for phase unit. Record the simulated V_{in} and I_2 in the sheet “Step 2.5” of the Excel file “Lab 3 – Multi-Stage Amplifier.xlsx”.
- 2.6 **Output Impedance:** Set the DC value of $I_{REF} = 91.0 \mu\text{A}$ and its AC value to $0 \mu\text{A}$. Set the DC value of V_2 to 0 V and the AC voltage of V_2 to $1 \mu\text{V}$. Conduct AC analysis to measure V_{in} and I_2 (taken from the negative terminal of C_2) in LIN with start frequency = 100 Hz, stop frequency = 200 Hz, and 11 frequency points in total. Choose REAL for magnitude unit and degree (DEG) for phase unit. Record the simulated V_{in} and I_2 in the sheet “Step 2.6” of the Excel file “Lab 3 – Multi-Stage Amplifier.xlsx”.

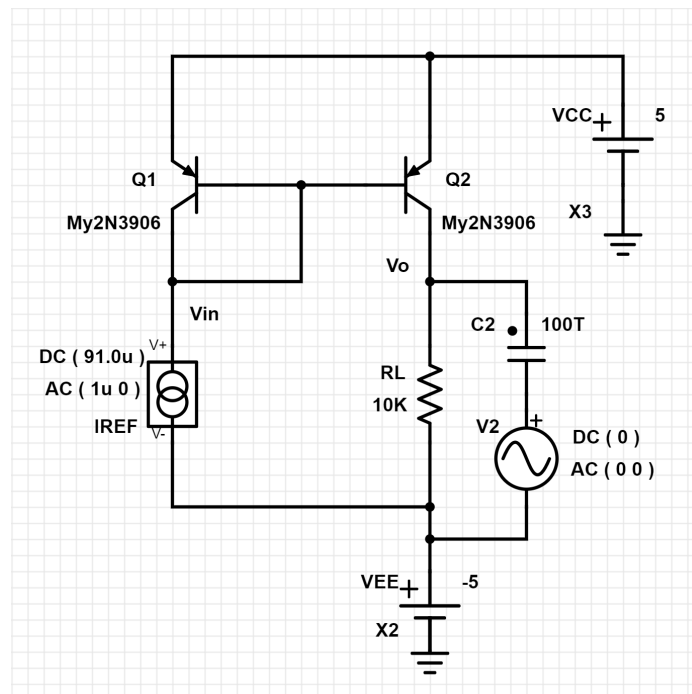


Fig. 3 Schematic diagram of the current mirror for the AC analysis

C. Questions for Part 1:

For the current mirror designed, answer the following questions with simulated data, and justify the simulation results.

Q3. (15 Points) (1) Based on Section 8.2.3 in the textbook, derive the relationship to express I_o as a function of I_{REF} . (2) Based on the simulation data obtained in Step 2.2, when I_{REF} is 0.1 mA, how is I_o compared with I_{REF} ? When I_{REF} is 1 mA, how is I_o compared with I_{REF} ? (3) Justify the observation between the theoretical prediction and the simulated result at I_{REF} is 0.1 mA and 1 mA, respectively.

Q4. (15 Points) (1) Based on the simulation data obtained in Step 2.5, what is the input impedance R_{in} looking from V_{in} toward the collector of Q1? What is the current gain A_i of the current mirror? (2) Based on the simulation data obtained in 2.6, what is the output impedance R_o of the current mirror looking into the collector of Q2? (3) Based on the information obtained in (1) and (2), draw the linear two-port network for the current mirror using its h -parameters.

Part 3: Differential Amplifier with a Current Mirror (CM) Load

A. Pre-lab Simulation

- 3.1 In [PartSim](#) (or [LTspice](#)), construct a differential amplifier, as shown in Fig. 4, using the current mirror (CM) load characterized in Part 1.
- 3.2 **Frequency Response:** Set the DC values of V_1 and $V_2 = 0$ V, and their AC amplitude 1 mV. For the differential-mode signal, set the phases of the AC signal V_1 and V_2 to be 0° and 180° , respectively, as shown in Fig. 4. In this setting, the differential-mode signal $v_{id} = V_1 - V_2 = 1$ mV $- (-1$ mV) = 2 mV. Conduct AC analysis for V_o in DEC with Start Frequency = 100 Hz, Stop Frequency = 100 kHz, and Total Points Per Decade = 101. Choose REAL for magnitude unit and degree (DEG) for phase unit. Record the measured $|V_o|$ and $\angle V_o$ in the sheet “Step 3.2” of the Excel file “Lab 3 – Multi-Stage Amplifier.xlsx”.

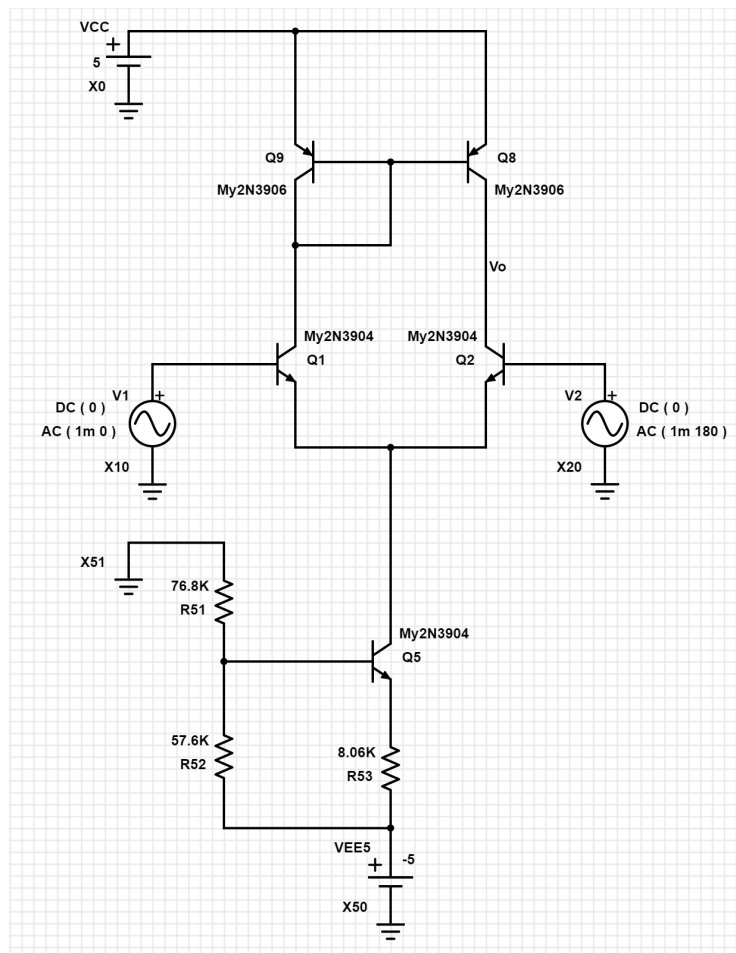


Fig. 4 Schematic diagram of the differential amplifier with a CM load for differential-mode analysis

B. In-lab Measurement

- 3.3 Use the port definition diagram of the AD2 shown in Fig. 5 when setting up your circuits.
- 3.4 Based on Fig. 4, construct the measurement setup for the differential amplifier with a current mirror load. **Tip:** Replace the two 8.25 k Ω resistors in Lab 2 with the current mirror.

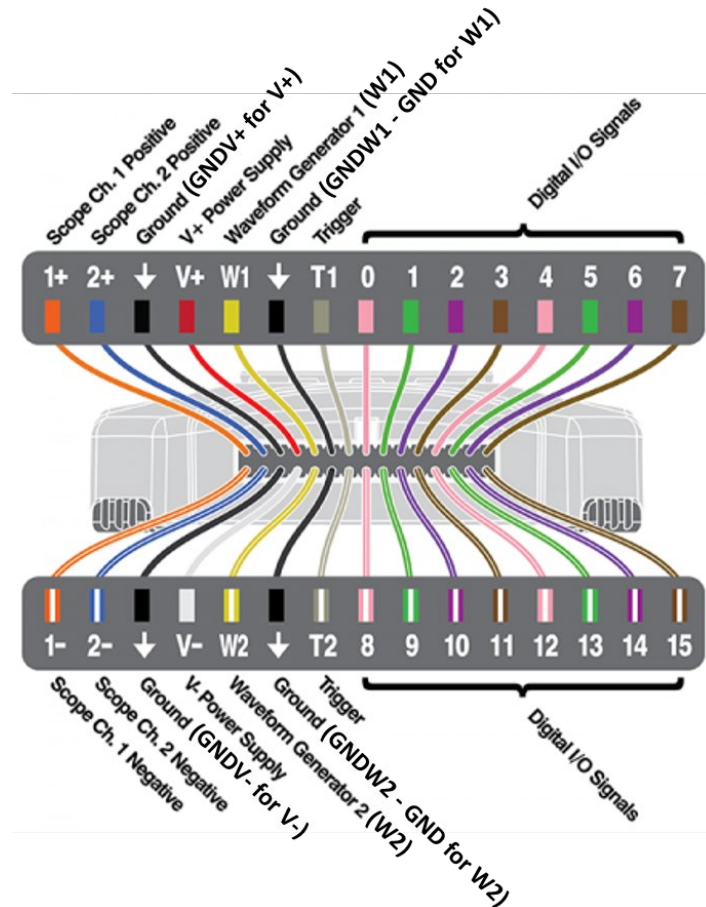


Fig. 5 Diagram for the port definition of an Analog Discovery 2 (AD2)

- 3.5 Use $V^+ = 5\text{V}$ for V_{CC} , $V^- = -5\text{V}$ for V_{EE} , Wavegen 1 (W1) for V_1 and Wavegen 2 (W2) for V_2 . Connect GNDV+, GNDV-, GNDW1, and GNDW2 to a common ground line.
- 3.6 **DC Offset Voltage:** Due to the finite β and Early effect of Q_8 and Q_9 , as described in (3.3) and (3.4), they result in a mismatch between the collector currents of Q_1 and Q_2 . We need to balance their DC currents by applying offset voltage to Q_2 (or Q_1). To find the required dc offset voltage, connect Scope Ch. 1 Positive (1+) to the collector of Q_1 and Scope Ch. 2 Positive (2+) to V_o (i.e., the collector of Q_2). In WaveForms, click Workspace, open the provided workspace script “Lab3_Step3.6.dwf3work” and press Run. This script will set the offset voltage of Wavegen 1 (W1) to 0 V and gradually change the offset voltage of Wavegen 2 (W2) until the DC voltages V_{C1} at the collector of Q_1 and V_o at the collector of Q_2 to be the same (or very close). Record the measured V_{C1} and V_o in the sheet “Step 3.6” of the Excel file “Lab 3 – Multi-Stage

Amplifier.xlsx". Calculate V_{BC8} of Q_8 by $V_{BC8} = V_{C1} - V_o$ to ensure V_{BC8} is larger than -0.4 V to have Q_8 work in the active region. If Q_8 does not work in the active region (e.g., $V_{C1} = 4.39$ V and $V_o = 4.93$ V), Q_8 and Q_9 do not function as a current mirror anymore.

- 3.7 **Differential-mode Voltage Gain:** Connect Scope Ch. 1 Positive (1+) to Wavegen 1 (W1), Scope Ch. 2 Positive (2+) to V_o (the collector of Q_2). In WaveForms, click Workspace, open the provided workspace script "Lab3_Step3.7.dwf3work", change the W2Offset value in the script to the value obtained in Step 3.6, and press Run. This script will enable both Channel 1 (W1) and Channel 2 (W2) and set their Type = Sine, Frequency = 100 Hz, Amplitude = 1 mV, Channel 1 (W1) Offset = 0 V, Channel 2 (W1) Offset = W2Offset, Symmetry = 50%, the Channel 1 (W1) Phase = 0° , and Channel 2 (W2) Phase = 180° . It will return the differential-mode gain A_{vd} in dB.
- 3.8 **Using Scopes:** Display the measurement results using the Scope function in WaveForms. Use Y Cursors to set their upper and lower peak values and use the Ref function to calculate the difference. Record the measured peak-to-peak amplitudes of Scope Ch. 1 Positive (1+) and Scope Ch. 2 Positive (2+) in the sheet "Step 3.8" of the Excel file "Lab 3 – Multi-Stage Amplifier.xlsx" to calculate the differential-mode voltage gain A_{vd} in dB. Copy and paste the screenshot of the measurement results to replace the one in the sheet "Step 3.8" of the Excel file "Lab 3 – Multi-Stage Amplifier.xlsx" to support your calculation. Make sure to capture the date and time of your PC in the screenshot.
- 3.9 **Multi-Stage Amplifier Gain:** Connect the output (the collector of Q_2 in Fig. 4) of the differential amplifier to the input (the base of Q_2 in Fig. 1) of the common-collector (CC) amplifier to form a multi-stage (or 2-stage) amplifier. Connect Scope Ch. 2 Positive (2+) to V_o (the emitter of Q_2 in Fig. 1). Run workspace script "Lab3_Step3.7.dwf3work" again with the same W2Offset value set in Step 3.7. Display the measurement results using the Scope function in WaveForms. Use Y Cursors to set their upper and lower peak values and use the Ref function to calculate the difference. Record the measured peak-to-peak amplitudes of Scope Ch. 1 Positive (1+) and Scope Ch. 2 Positive (2+) in the sheet "Step 3.9" of the Excel file "Lab 3 – Multi-Stage Amplifier.xlsx" to calculate the differential-mode voltage gain A_{vd} in dB. Copy and paste the screenshot of the measurement results to replace the one in the sheet "Step3.9" of the Excel file "Lab 3 – Multi-Stage Amplifier.xlsx" to support your calculation. Make sure to capture the date and time of your PC in the screenshot.
- 3.10 Disconnect the circuit from the power supply V_{CC} , but keep the rest of the differential amplifier connected. We will use it again in Lab 4 when we design a directly coupled operational amplifier.

C. Questions for Part 2:

For the differential amplifier designed, answer the following questions with simulated and measured data, and discuss any discrepancy between the simulation and measurement results.

Q5. (15 Points) (1) Based on the simulation data obtained in Step 3.2, what is the voltage gain A_d in dB for the differential-mode signal? (2) Did you observe any mismatch in Step 3.6? If yes, how much offset voltage did you apply at V_2 ? (3) Compare your simulated result with the measured result obtained in Step 3.8.

Q6. (10 Points) Estimate its upper 3-dB frequency f_H (i.e., the frequency at which the amplitude becomes $1/\sqrt{2} = 0.707$ of its low-frequency value or the phase changes 45°).

Q7. (10 Points) Compare the upper 3-dB frequency f_{3dB} of this differential amplifier with a current mirror load with that of the differential amplifier using resistive loads obtained in Q8 of Lab 2. Why the differential amplifier with the current mirror load has smaller f_{3dB} ?

Q8. (10 Points) What are the gain-bandwidth products (GBW) in Hz of the two differential amplifiers with the current mirror load and the resistive load, respectively?